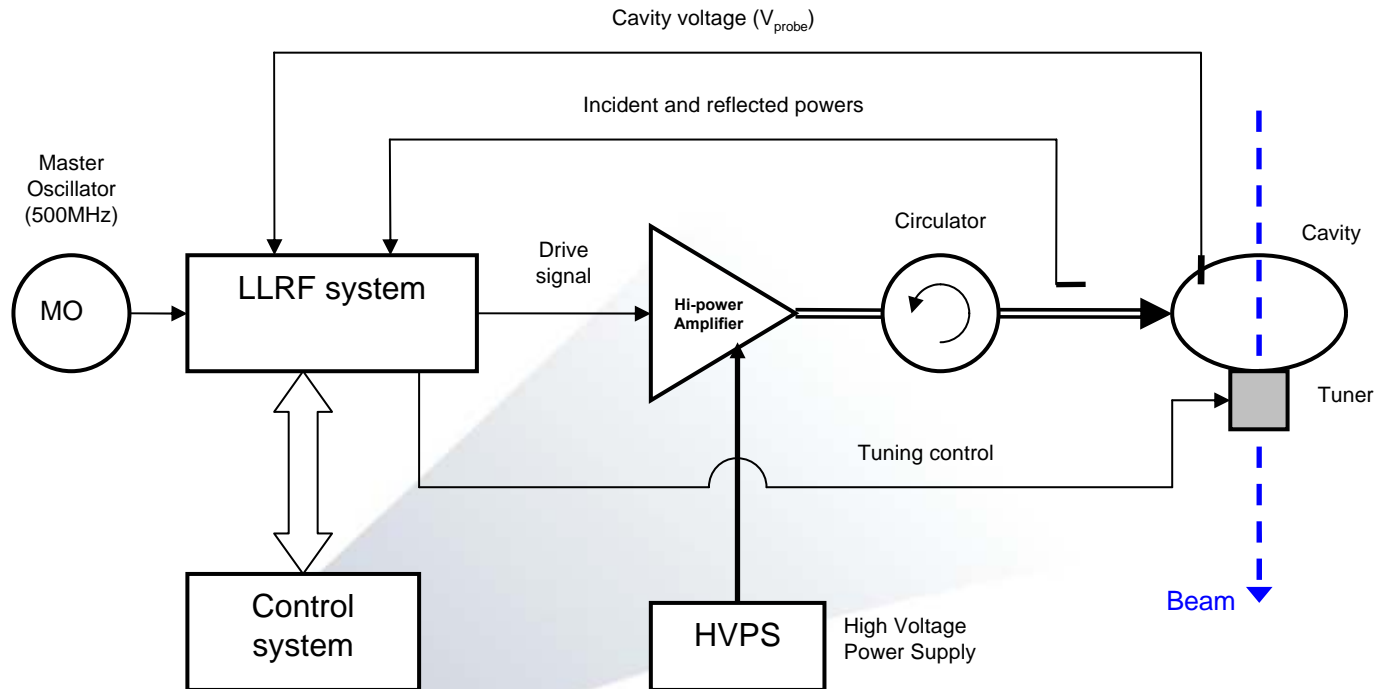


# Low Level RF of ALBA

(A preliminary study)

Hooman Hassanzadegan

## General view of the RF system




**The task of the LLRF is the regulation of the amplitude, frequency and phase of the RF wave.**


## LLRF - hardware

- ❑ Sensors for the incident, reflected and cavity power ( $P_{inc}$ ,  $P_{refl}$ ,  $P_{probe}$ )
- ❑ The required hardware for the isolation and amplification of the RF signals
- ❑ The required Digital / Analog circuits for regulation, interfacing, ADC, DAC, signal processing, etc.
- ❑ Drive power amplifier
- ❑ PIN diode
- ❑ Master oscillator
- ❑ Other modules including auxiliary power supplies, PLL, Interlock, etc.

# Amplitude and phase regulation loops

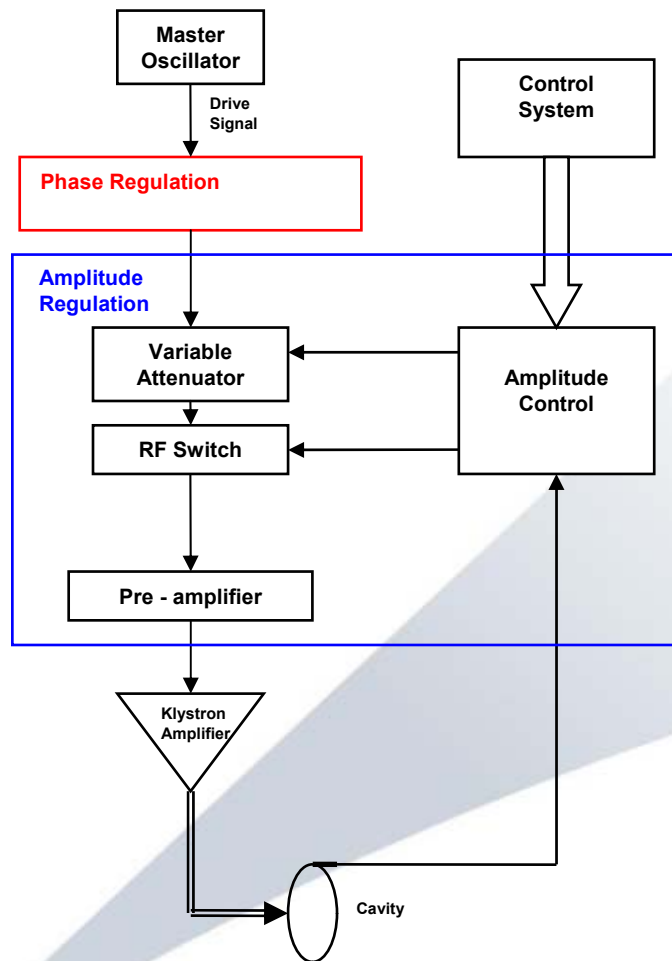

a) Amplitude Regulation

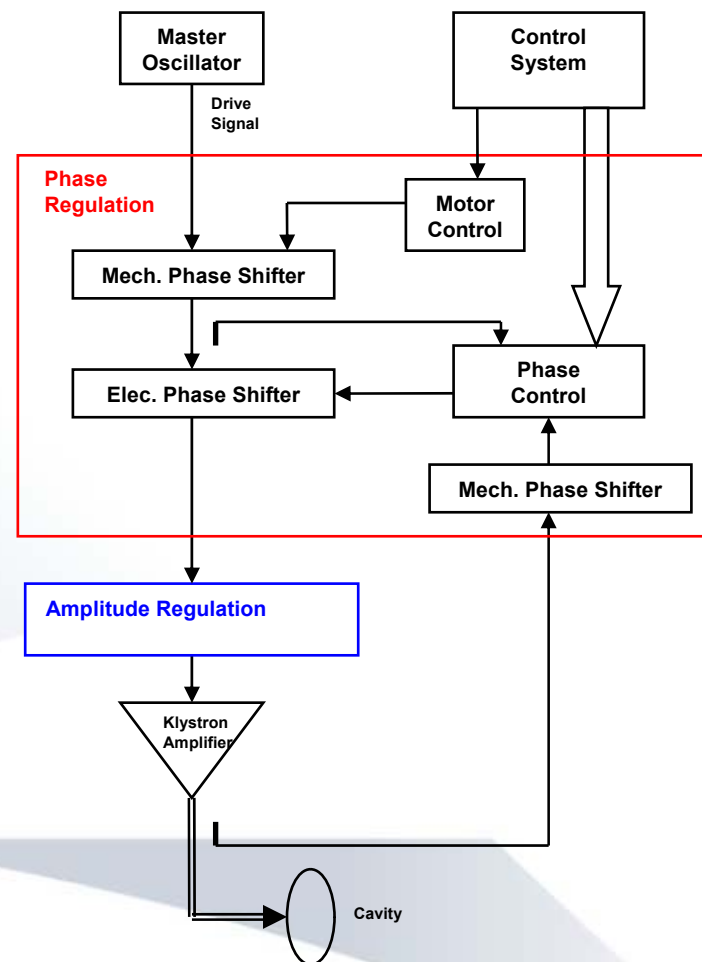


b) Phase Regulation

# I-Q demodulator and rotation matrix

Demodulation:

$$V(t) = I \cdot \cos(\omega t) + Q \cdot \sin(\omega t)$$
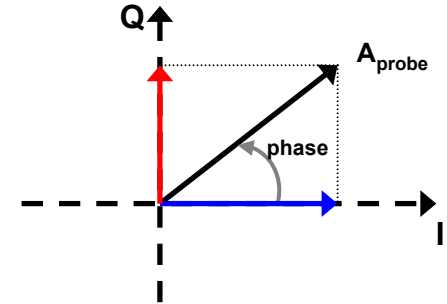
$$\begin{cases} I = A_{probe} \times \cos(\varphi_{probe} - \varphi_{MO}) \\ Q = A_{probe} \times \sin(\varphi_{probe} - \varphi_{MO}) \end{cases}$$




Modulation:

$$A_{probe} = \sqrt{I^2 + Q^2}$$

$$\varphi_{probe} - \varphi_{MO} = \arctan 2(Q/I)$$

Rotation matrix:

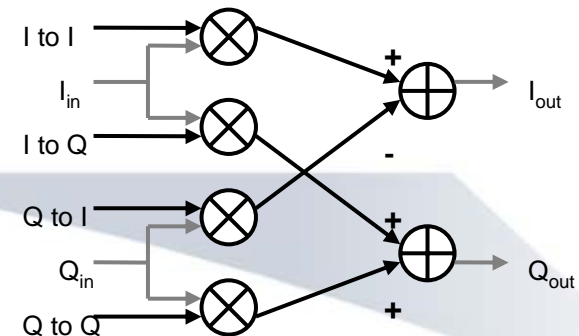
$$\begin{bmatrix} I_{out} \\ Q_{out} \end{bmatrix} = A \begin{bmatrix} \cos\theta & -\sin\theta \\ \sin\theta & \cos\theta \end{bmatrix} \times \begin{bmatrix} I_{in} \\ Q_{in} \end{bmatrix}$$




## General suggestions for ALBA LLRF

- **I-Q demodulation is more favourable, because two identical regulators will be used acting on baseband signals with wider phase control range compared to the traditional amplitude-phase loops.**
- **It's more desirable to use digital electronics which provides more flexibility, possibility of future changes by the software, better diagnostics and higher functionality compared to analog electronics.**
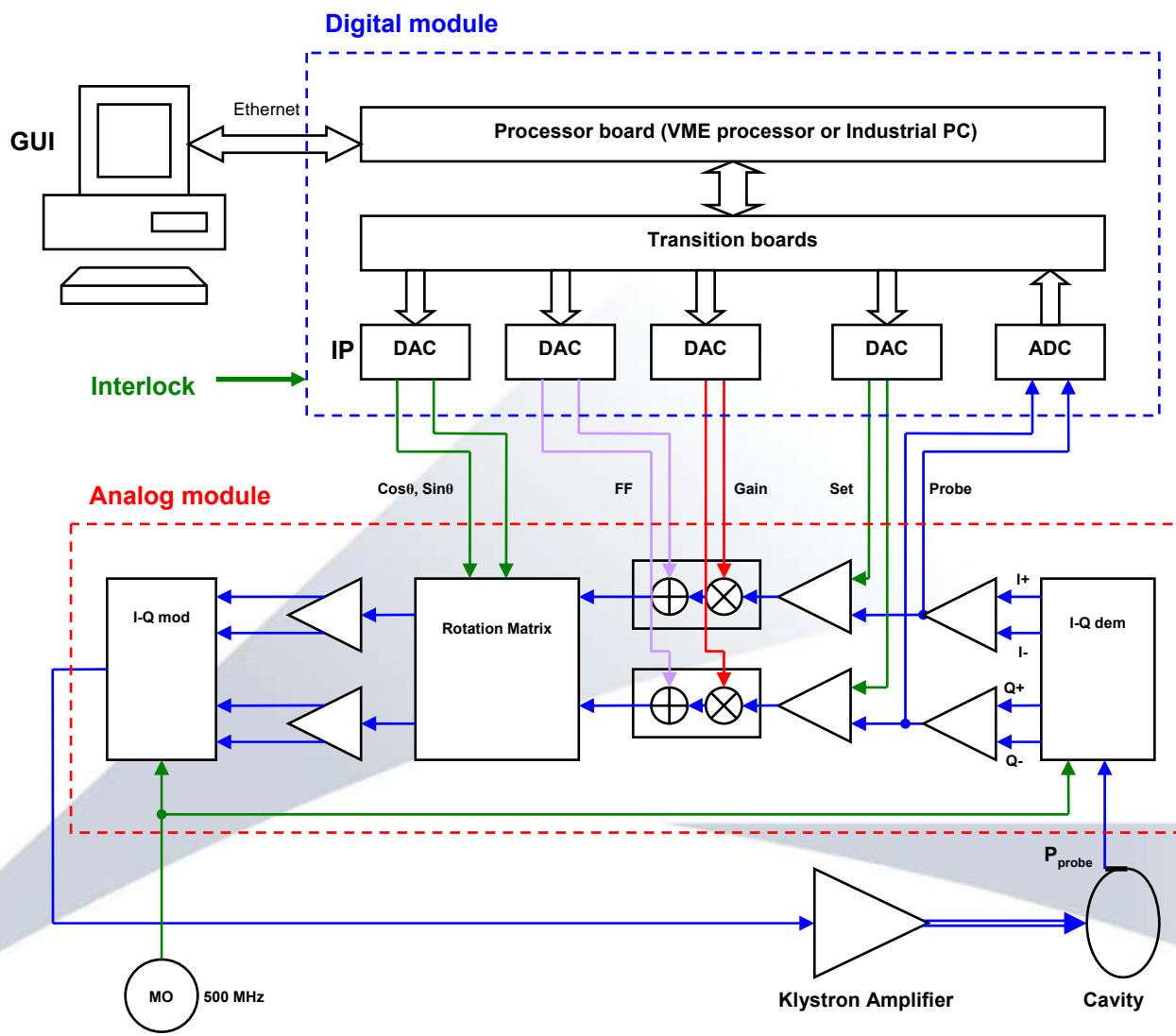
# Amplitude / phase control (analog and digital)




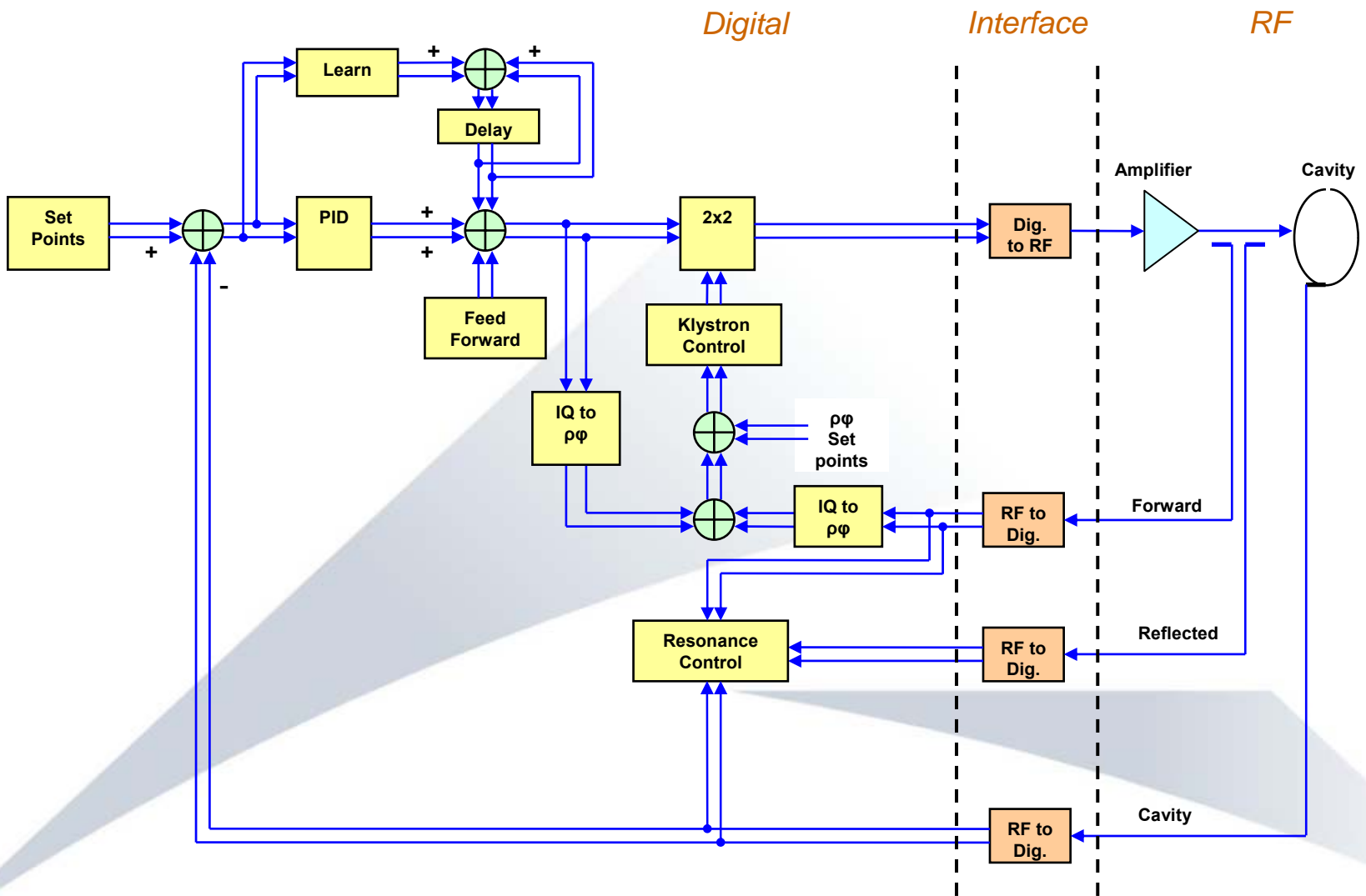
# Amplitude / phase control (all digital)





## Tuner control

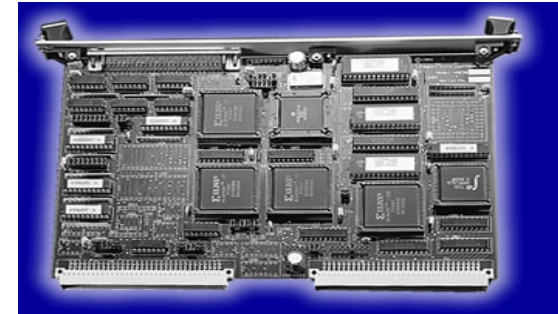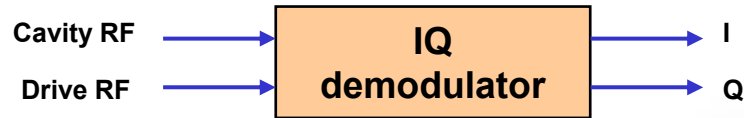

### Cavity tuner control:

- An IQ demodulator detects the phase difference between the drive RF and the actual cavity voltage
- The LLRF system drives the phase using the relation  $\text{Arctan}(Q/I)$
- The LLRF drives the cavity to maintain the desired phase difference

## Inputs / Outputs for LLRF controls

### Cavity voltage control inputs:

1. Reference RF
2. Cavity Voltage
3. Cavity In-phase setpoint (FB)
4. Cavity Quadrature setpoint (FB)
5. IQ regulator gains
6. Cavity In-phase setpoint (FF)
7. Cavity Quadrature setpoint (FF)
8. Rotation matrix parameters

### Cavity voltage control outputs:

1. Power amplifier drive
2. Cavity voltage In-phase monitor
3. Cavity voltage Quadrature monitor

### Cavity tuner control inputs:

1. Cavity voltage
2. Derive RF

### Cavity tuner control outputs:

1. Cavity tuning In-phase (I)
2. Cavity tuning Quadrature (Q)

**Electrical and performance specifications of the Input / Output signals still have to be defined.**


# The first step – IQ demodulator

- We'll need it with both Digital and Analog Reg.
- Detailed design is available
- Comparably easy to build
- Can be tested with a function generator




50 MHz–1000 MHz  
Quadrature Demodulator  
**AD8348**

**FEATURES**  
 Integrated I/Q demodulator with IF VGA amplifier  
 Operating IF frequency 50 MHz to 1000 MHz  
 (3 dB IF BW of 500 MHz driven from  $R_s = 200 \Omega$ )  
 Demodulation bandwidth 75 MHz  
 Linear-in-dB AGC range 44 dB  
**Third order intercept**  
 IIP3 +28 dBm @ min gain ( $F_{IF} = 380$  MHz)  
 IIP3 -8 dBm @ max gain ( $F_{IF} = 380$  MHz)  
**Quadrature demodulation accuracy**  
 Phase accuracy 0.5°  
 Amplitude balance 0.25 dB  
**Noise figure 11 dB @ max gain ( $F_{IF} = 380$  MHz)**  
 LO input -10 dBm  
 Single supply 2.7 V to 5.5 V  
**Power-down mode**  
 Compact 28-lead TSSOP package

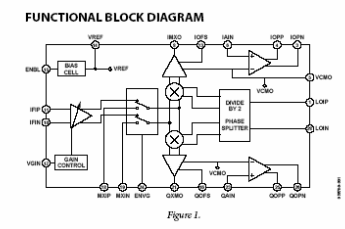

Optionally, the IF VGA can be disabled and bypassed. In this mode, the IF signal is applied directly to the quadrature mixer inputs via the MXIP and MXIN pins.

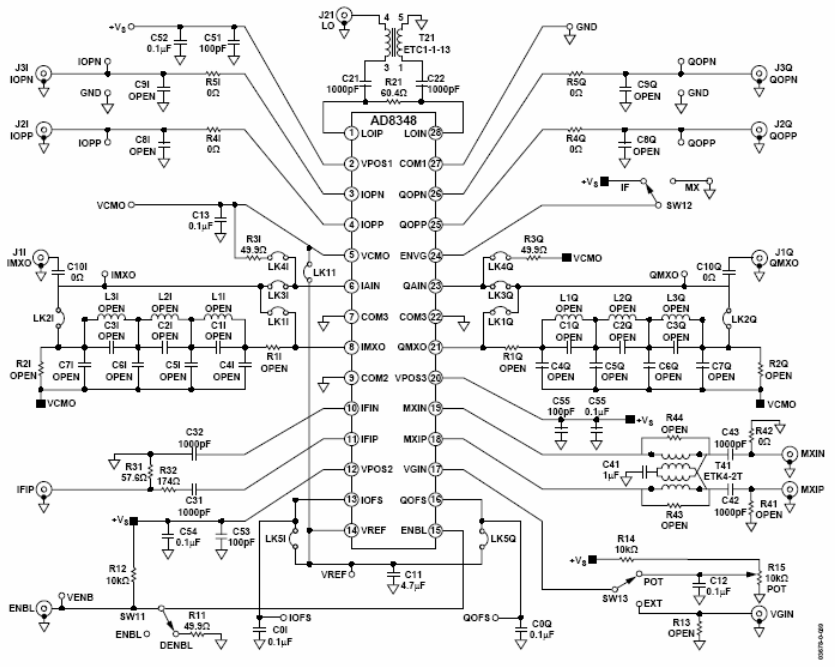**APPLICATIONS**  
 QAM/PSK demodulator  
 W-CDMA/CDMA/GSM/NADC  
 Wireless local loop  
 LMDS



## The next steps

1. I-Q demodulator (AD3343 from Analog Devices)
  - Can be designed and made at CELLS
  - Test with a function generator
2. **Other parts of the “Analog module”**
3. **ADC, DAC and processor boards (“Digital Module”)**
  - Off the shelf, but still need programming
  - will be done in collaboration with the Control Group
4. **Test with simulated system**
5. **Interfacing with the control system and GUI**
  - Will be done mainly by the Control Group
6. **Commissioning and trouble-shooting**