



CLUSTER OF RESEARCH INFRASTRUCTURES
FOR SYNERGIES IN PHYSICS



ESLS-RF


BESSY, September 18-19 , 2013

First power results of the cavity combiner

Michel Langlois, ESRF, SSA R&D


Pierre Barbier, ESRF, SSA R&D

Remember ?

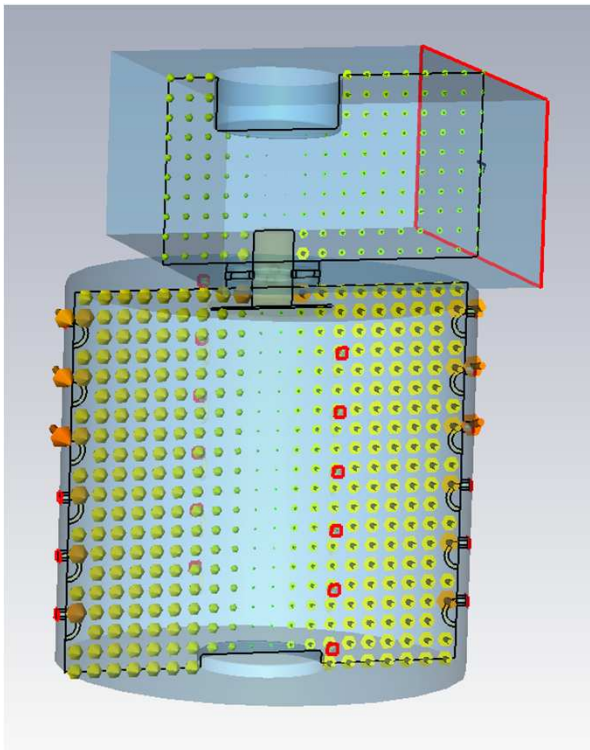

H field

E010 mode

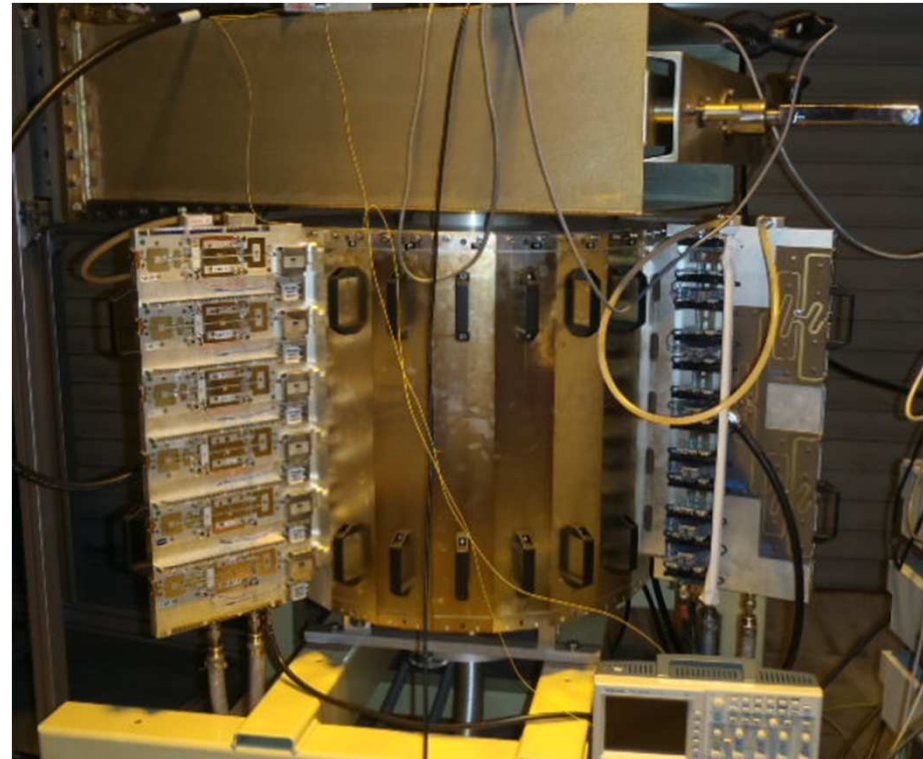


10 kW prototype:

- Only 3 active water cooled wings:
3 x 6 modules with up to 700 W /
module

RF drive split

As there are 6 modules per wing, the input signal on each wing has to be split in 6 with equal amplitude and phase.

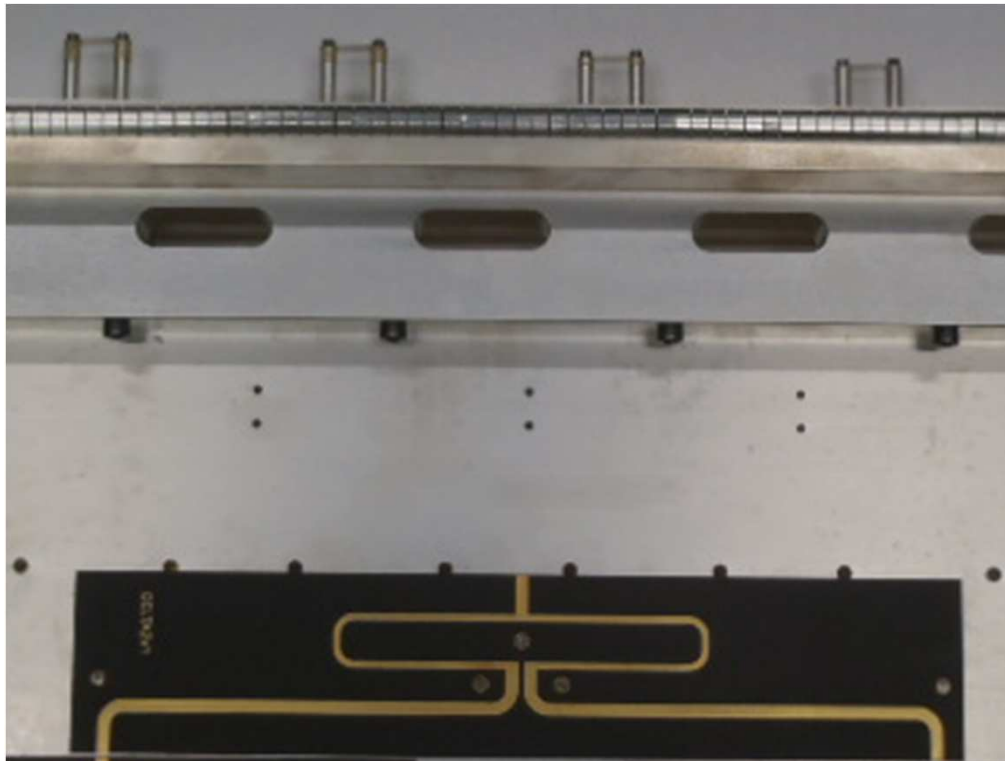
The first stage is a Wilkinson delta .It divides the signal by two.



V1 is too large and interferes with the holes for the drain DC filters.

item	S21 dB	S31 dB	Δ max dB	ϕ (S21) °	ϕ (S31) °	Δ max °	S11 dB	S32 dB
DELTA A	-3.11	-3.1	0.01	148.5	148.7	0.2	-23.6	-28.5
DELTA B	-3.11	-3.11	0	148.9	149	0.1	-23	-27.9
DELTA C	-3.11	-3.11	0	148.9	149.3	0.4	-22.4	-28.2

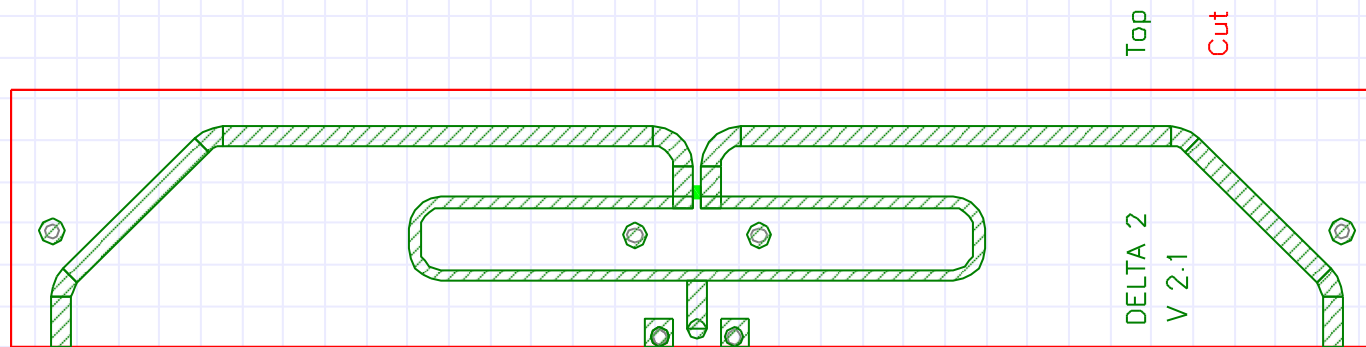The approximate input match is partly due to the N connection.



The N connector stands on a spacer grounded with via holes. It does no longer interfere with the DC distribution.

RF drive split

The second stage is a Wilkinson divider with 3 branches, star connected.



The resistors are not shown on this picture.



RF drive split


Overall splitter data

	Si1	Δ_{\max}	$\phi(\text{Si1})$	Δ_{\max}	S11	Sij
	dB	dB	°	°	dB	dB
wing A	-7.94	0.06	-25.1	1.3	-23.1	-26
wing B	-7.95	0.09	-24	1.2	-23	-26.3
wing C	-7.95	0.04	-24.2	0.9	-22.7	-26.1

NB: $-7.95\text{dB} = 1/6.2$

• RF modules : the bet

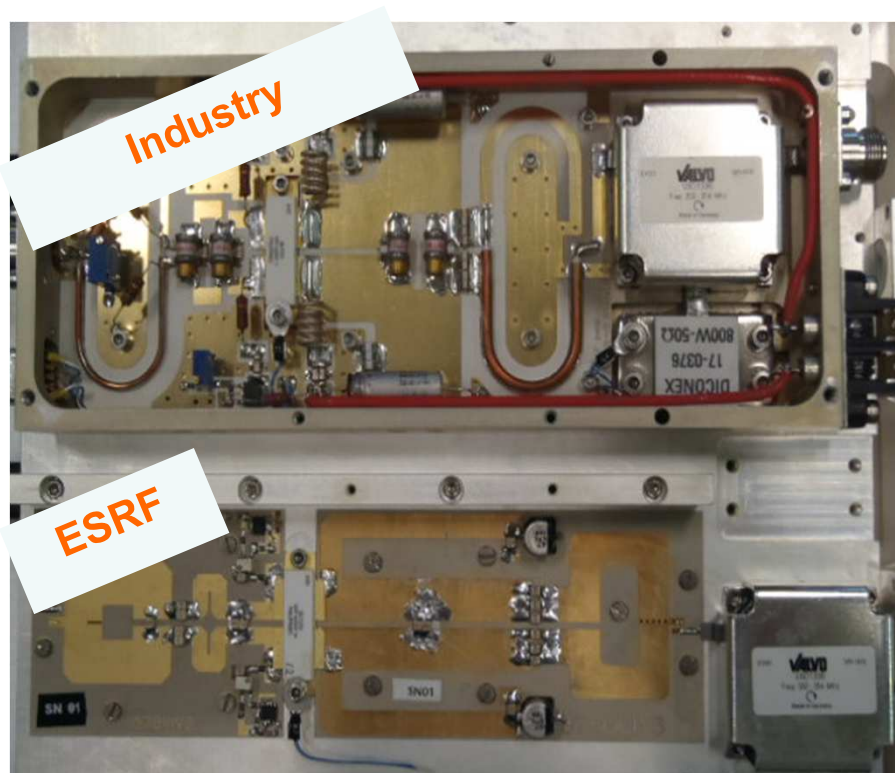All trimmers were avoided, making tuning very difficult. The idea was to suppress hand made components, thus making tuning unnecessary.



- Printed circuit baluns
- RF drain chokes replaced with “quarter wave” transmission lines.
- Very few components left, all of them SMD and prone to automated manufacturing in Europe.
- The biggest bet was the reproducibility of the push-pull MOSFET.


BILL OF MATERIAL:
(quantity 22 *6 modules)
Circulator and MOSFET
included

€€€ 390 €€€€!


- RF modules : the bet

All modules could be tested separately after being installed on their wing.

Gain histogram

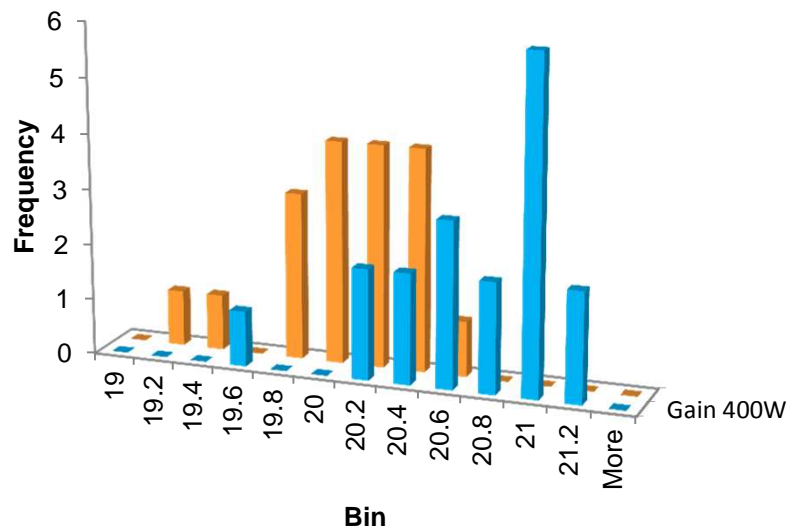

Phase histogram

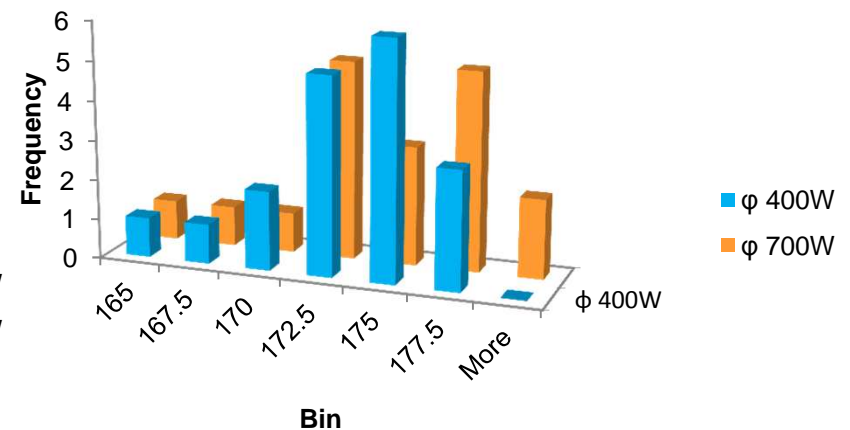


	Average gain	σ	Average phase	σ
400W	20.61	0.38	171.9	3.5
700W	19.95	0.39	173.2	4




- RF modules : the bet

Efficiency histogram

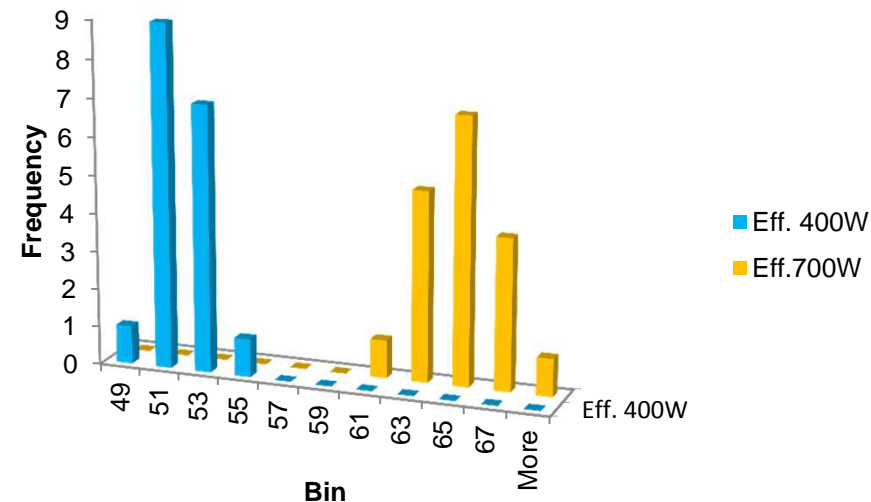

	Average eff.	σ
400W	50.8	1.5
700W	64.1	1.7


- RF modules : the bet

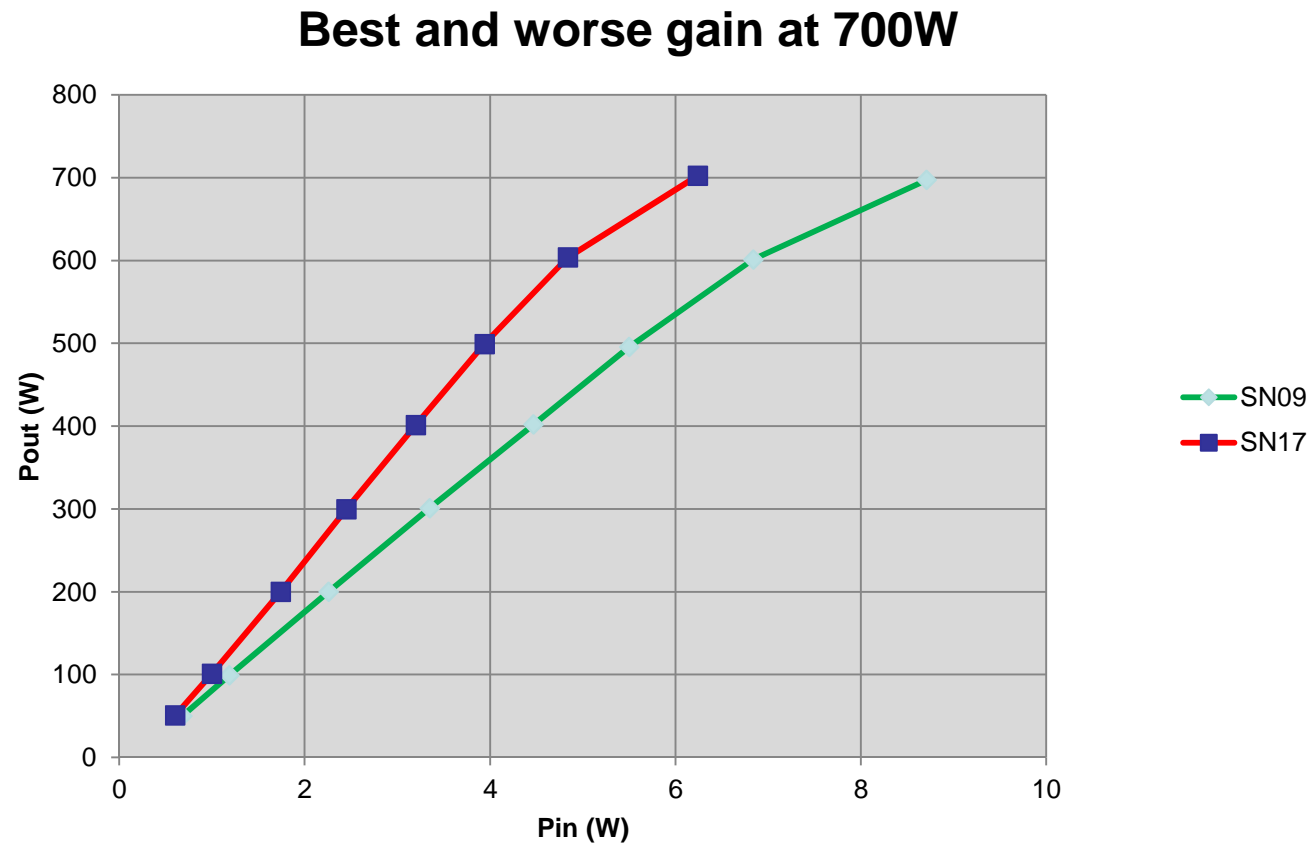


- **Circulators (the same as implemented by Soleil in ESRF amplifiers)**



S21 amp. histogram

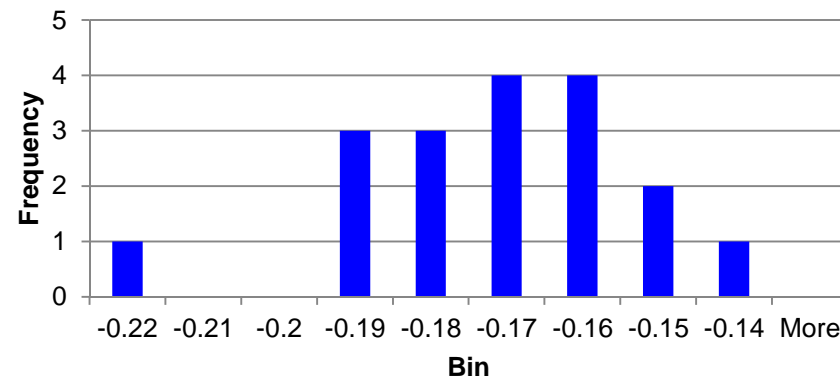


S21 phase histogram

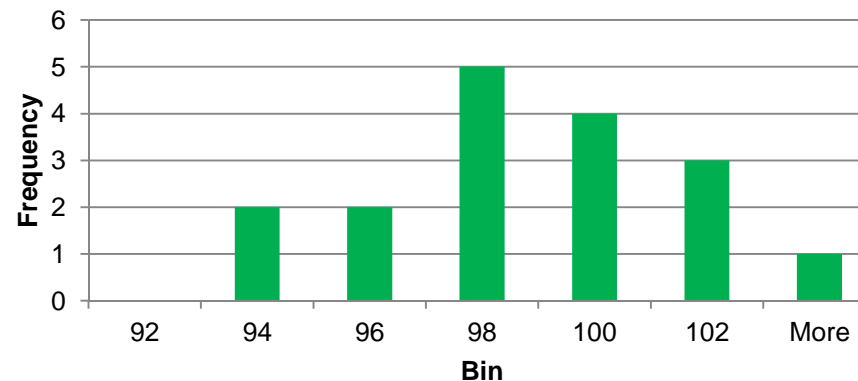

• The complete wing

4 parameters can be measured for each RF module:

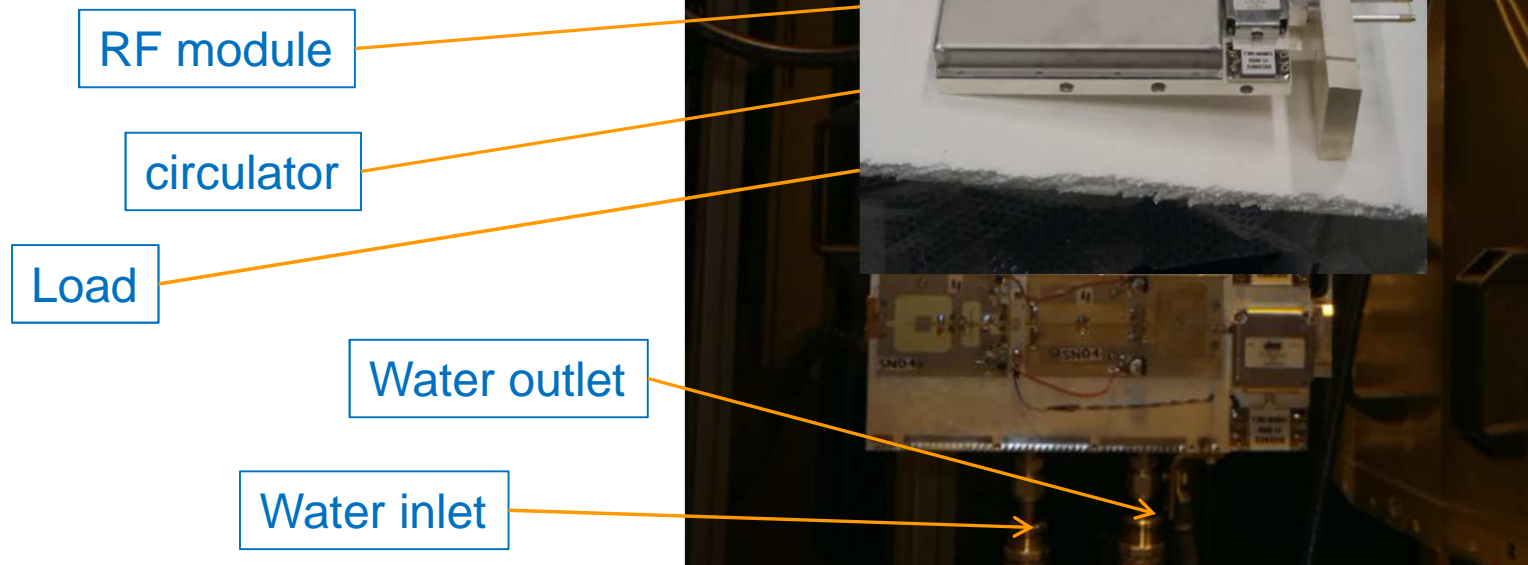- Both drain currents
- Transistor sole temperature
- Load case temperature



- **DC supplies, pre-amp, cooling**

Water temperature and flow indicators

Interlocks

Pre-amp

3 DC supplies 50V/140A



Cooling skid

Pump


Heat exchanger

Flow meter

Temperature sensors




- Input coupling of the cavity combiner

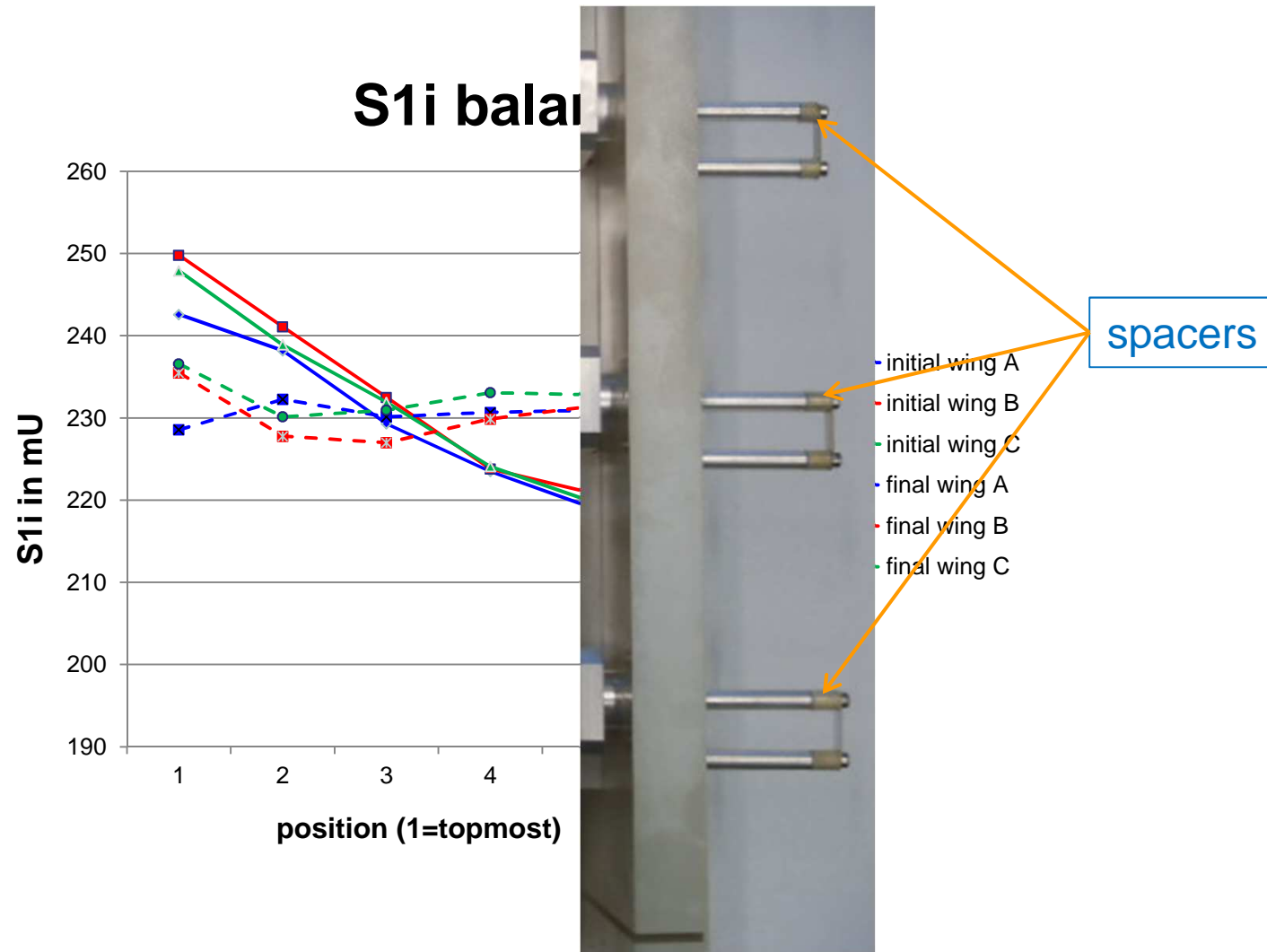

- RF results

Ampli vs. "average" module

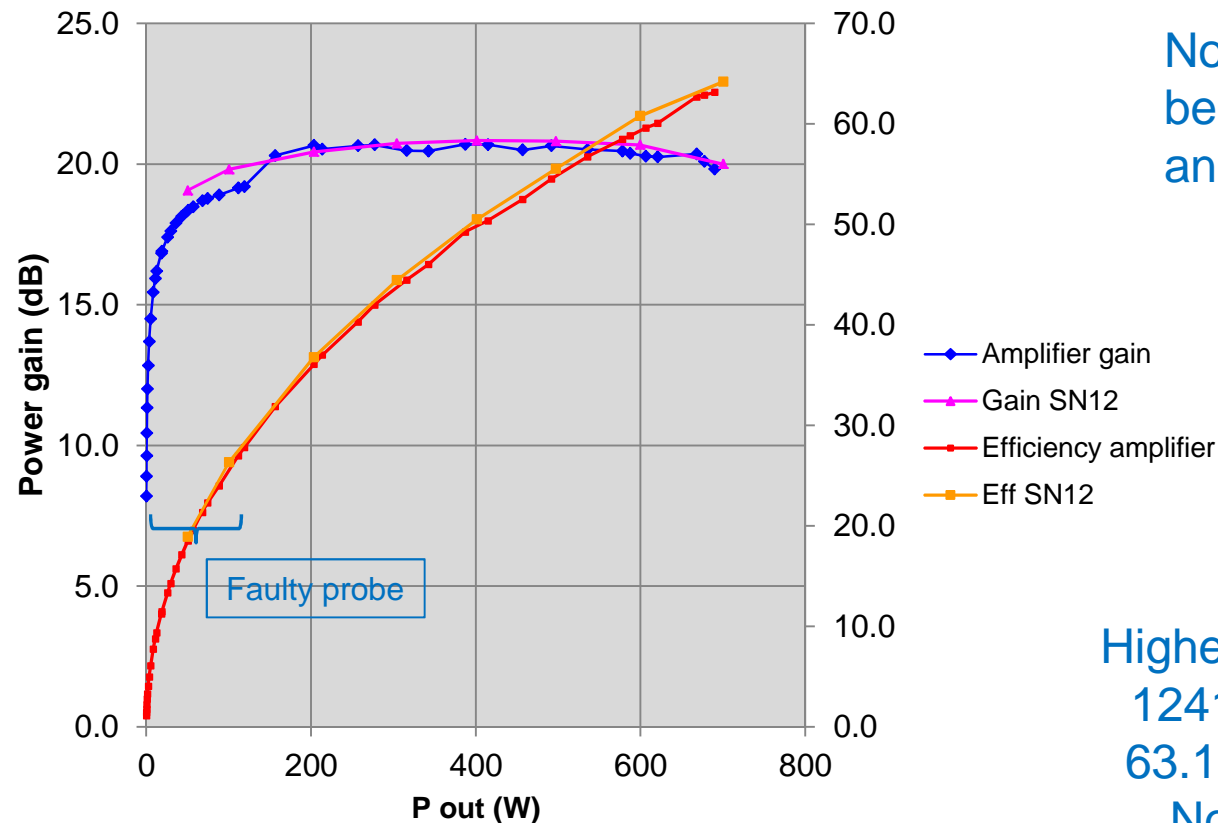


No big difference in the behavior of the amplifier and an "average" module.

Highest value reached:
 $12417W = 690W \cdot 18$
63.1% drain efficiency
No failure so far!

• RF results (2)

Load and sole temperatures

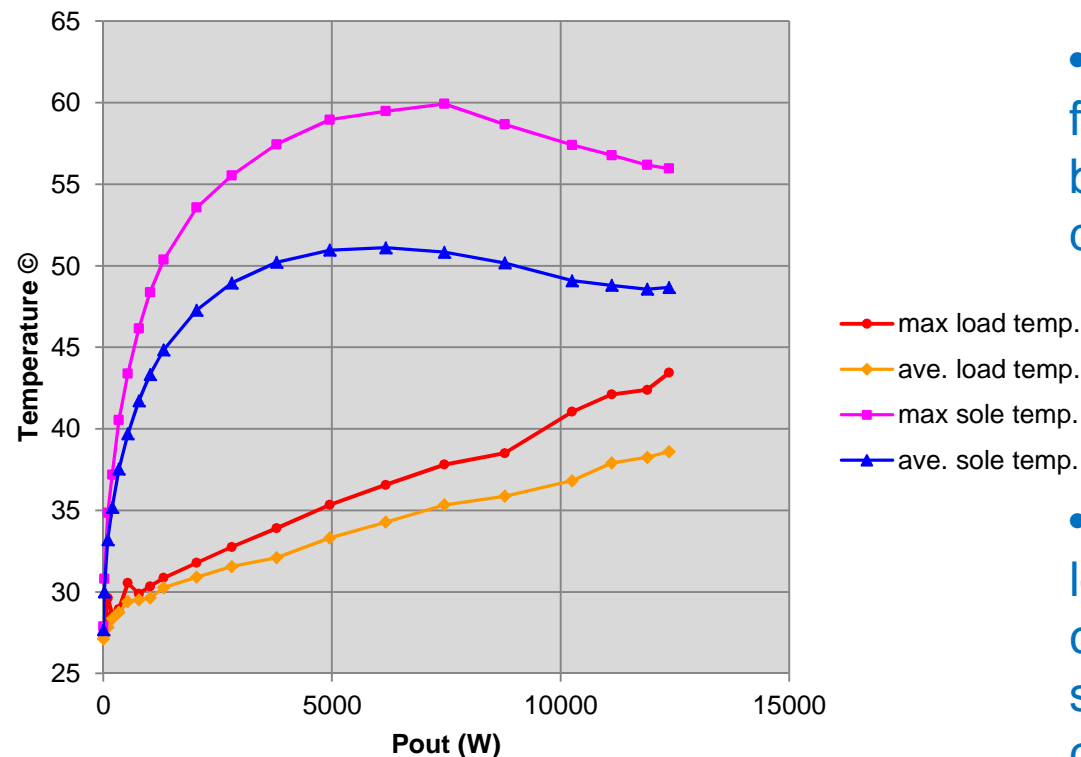

- The transistor temperature follows the usual class B behavior, with maximal dissipation around half power.

- Some power is wasted in the loads, probably due to the cumulated discrepancies of splitters, modules, circulators and cavity input loops.

An aerial night photograph of the European Synchrotron Radiation Facility (ESRF) in Grenoble, France. The large, circular, white-roofed building is illuminated from within, and its central area is a green field. The surrounding city of Grenoble is visible with its lights, and the French Alps are in the background under a twilight sky. The text "Thank you !" is overlaid in yellow.

Thank you !

Special thanks to my colleague
from the ESRF RF group and to
Hans Kartmann (NXP)